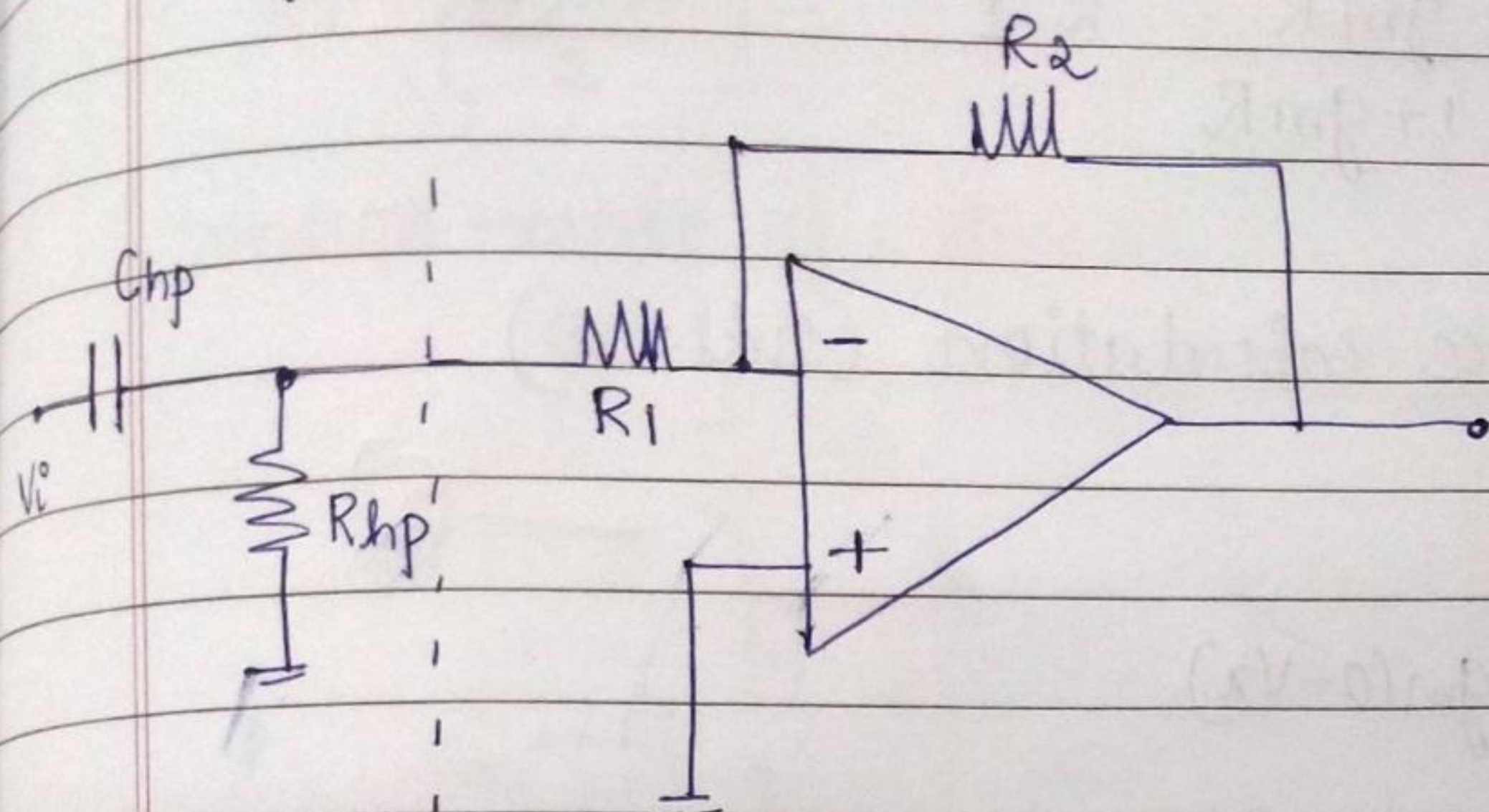


(1) Design a high pass filter with inverting amplifier.





Design: $XY = -\frac{R_2}{R_1}$ — (2)

$f_H = \frac{1}{2\pi C_{hp} R_{hp}} = 150 \text{ Hz}$ — (2)

choose R_{hp} , C_{hp} appropriately. — (2)


(2) Source follower

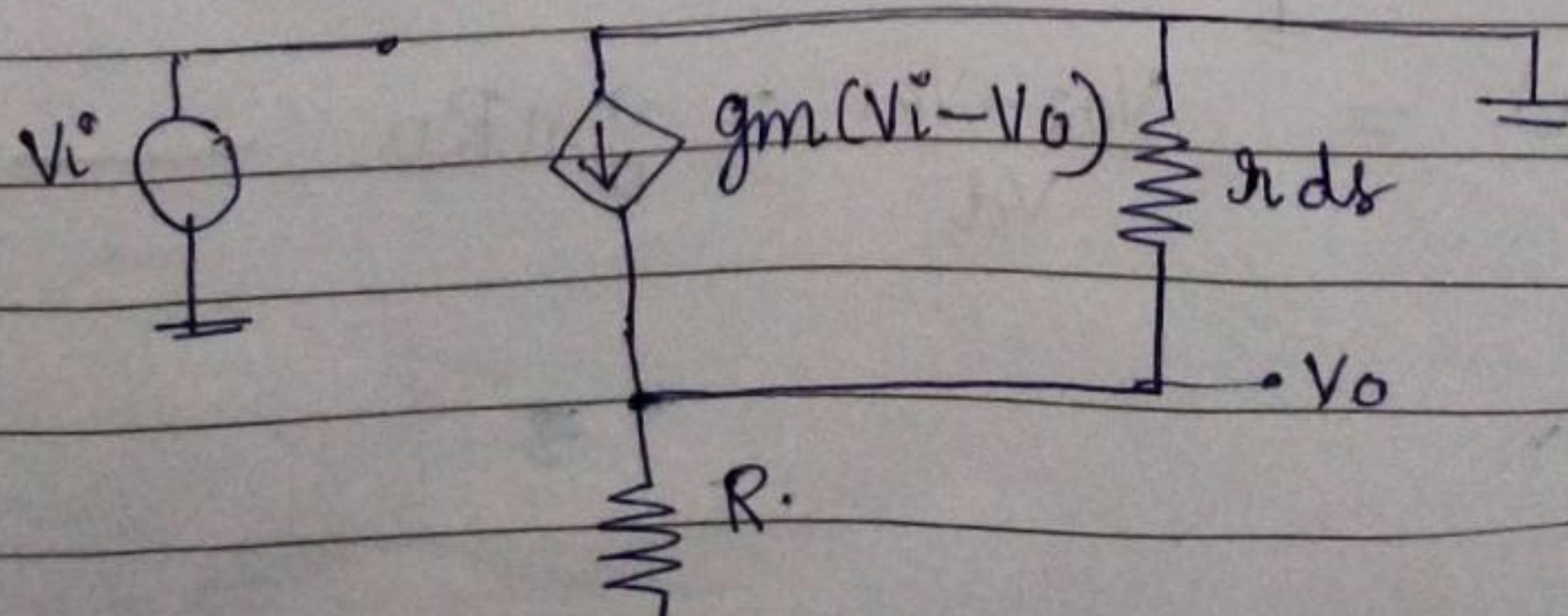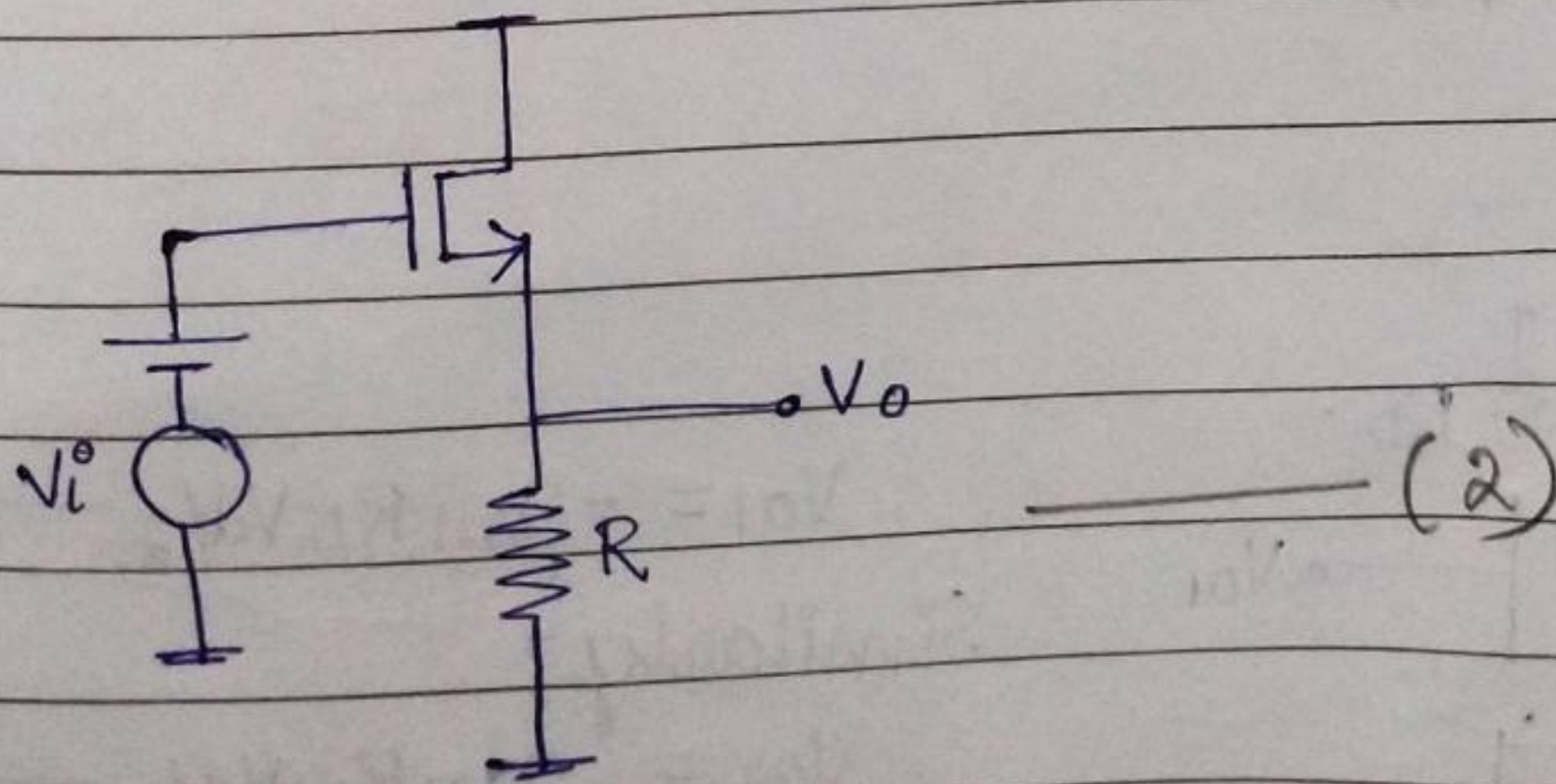

small signal gain (assuming $\lambda=0$) i.e. $r_{ds}=\infty$

$$A_v = \frac{V_o}{V_{in}} = \frac{g_m R}{1 + g_m R} \approx 1$$

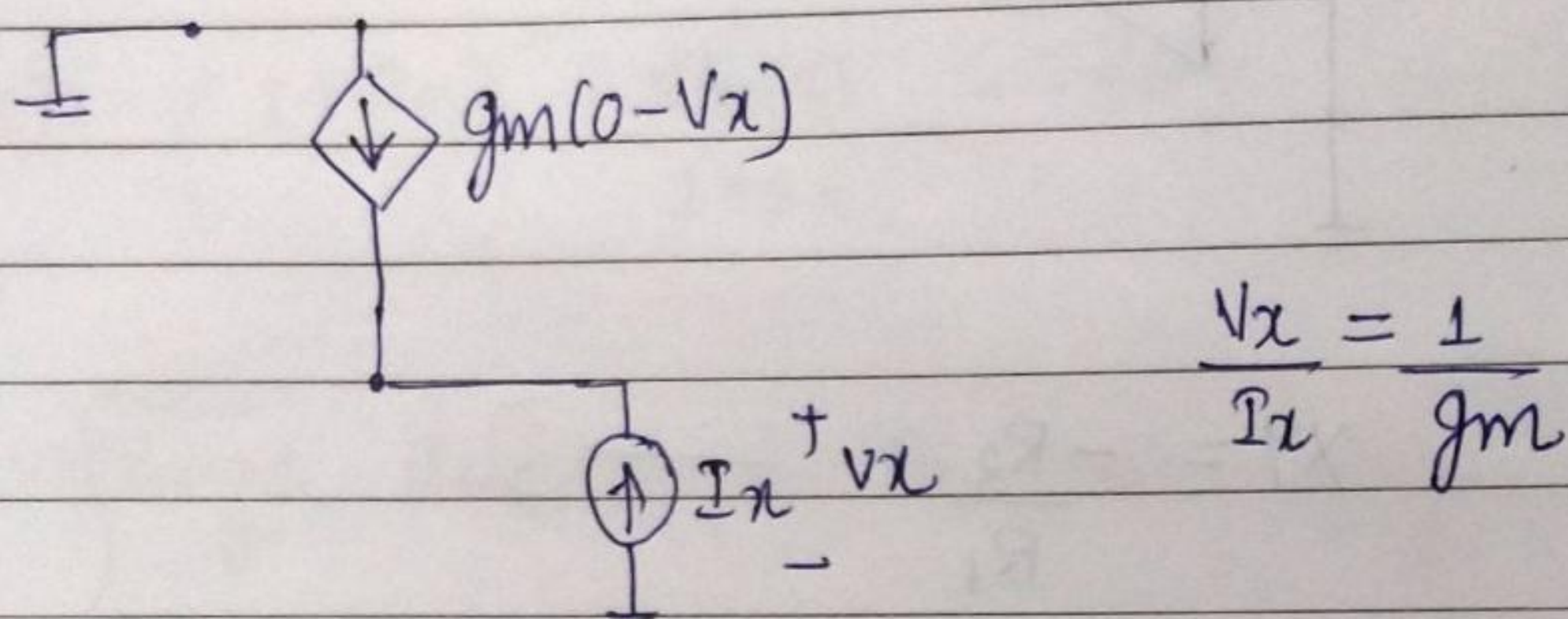o/p impedance calculation ($r_{ds}=\infty$)




o/p impedance with load $R = R \parallel \frac{1}{g_m}$

(3) Differential gain calculation. (A_d) $\rightarrow 8 \checkmark$

$$\rightarrow V_d = (V_{i^+} - V_{i^-})$$

The source voltages at small signal gnd for differential i/p.

Half circuit

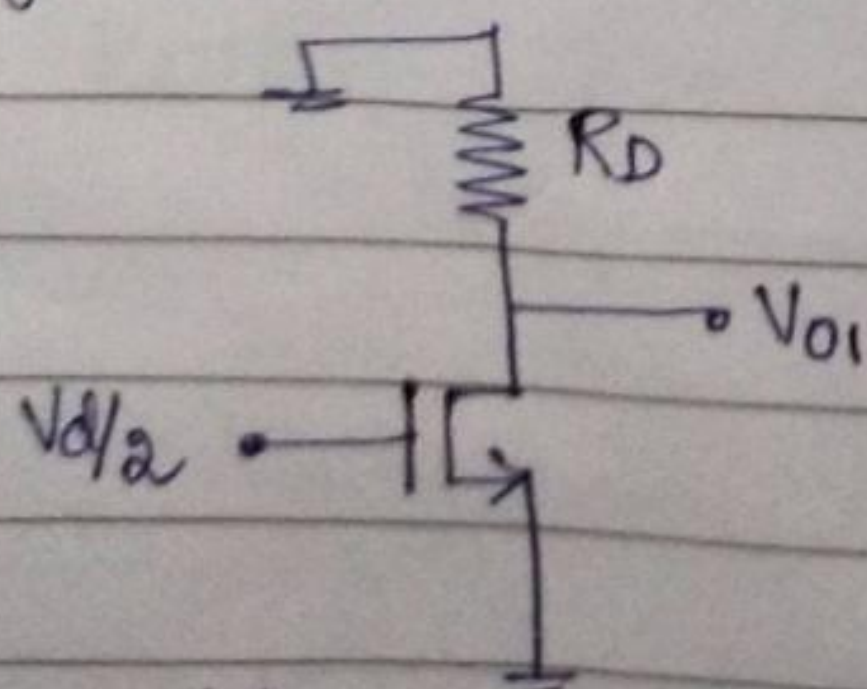

$$V_{o1} = -g_{m1} R_D V_d/2 \quad \text{--- (i)}$$

Similarly


$$V_{o2} = g_{m1} R_D V_d/2 \quad \text{--- (ii)}$$

$$A_d = \frac{V_{o2} - V_{o1}}{V_d} = g_{m1} R_D \quad \text{--- (3)}$$

common-mode gain.

$$V_{cm} = \left(\frac{V_{i^+} + V_{i^-}}{2} \right)$$

common-mode eq. circuit

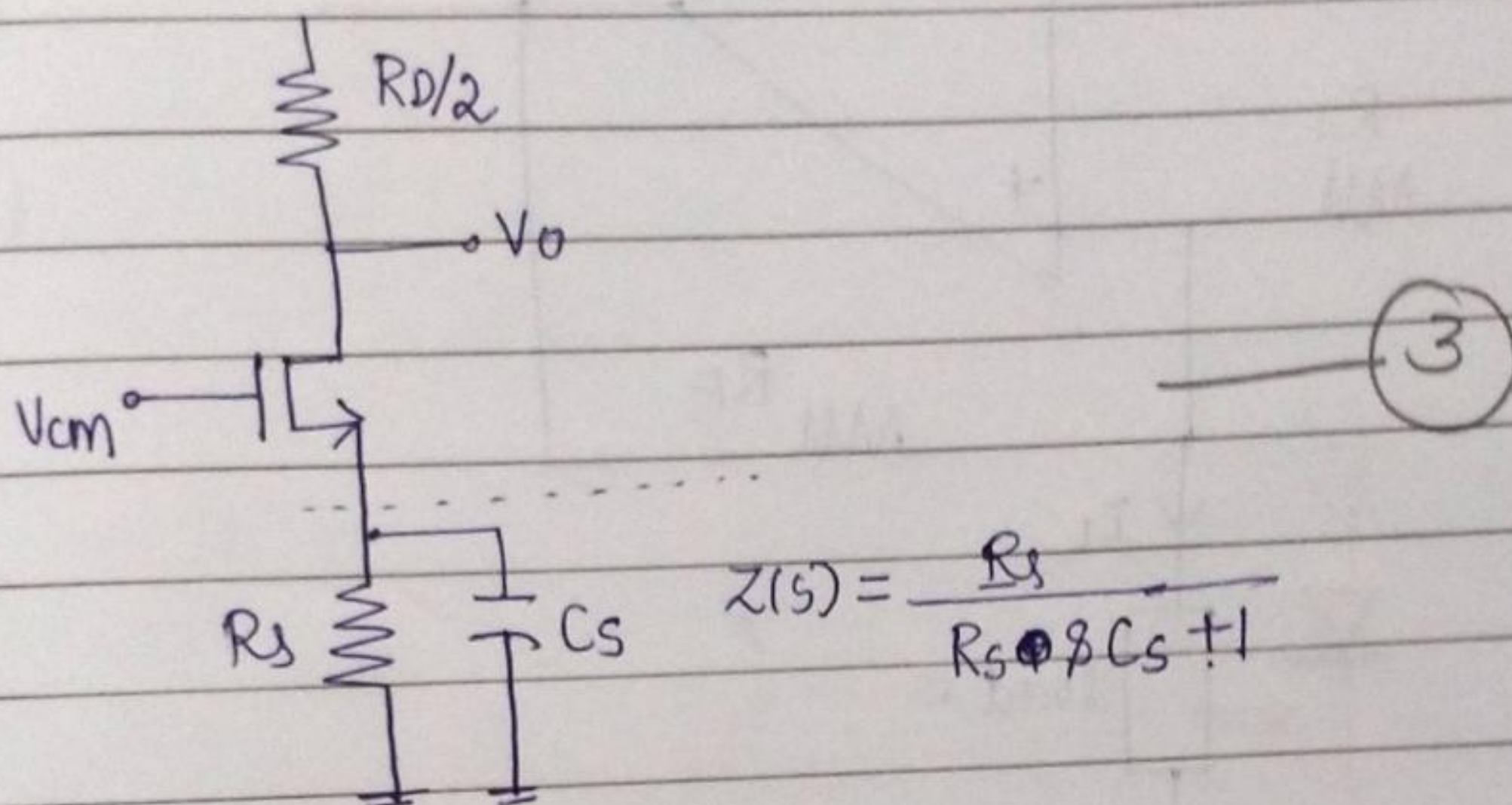

$$A_{cm} = \frac{-g_m R_D/2}{1 + g_m Z(s)}$$

$$CMRR = \frac{|A_d|}{|A_{cm}|} \quad \text{--- (2)}$$

obs :- \rightarrow (3)

3 (a) if $C_s = 0$, $Z(s) = R_s$ $|A_{cm}| = \frac{g_m R_D/2}{1 + g_m R_s}$

if $C_s = \infty$, $Z(s) = 0$ $|A_{cm}| = g_m R_D/2$

as C_s value increases CMRR decreases.