
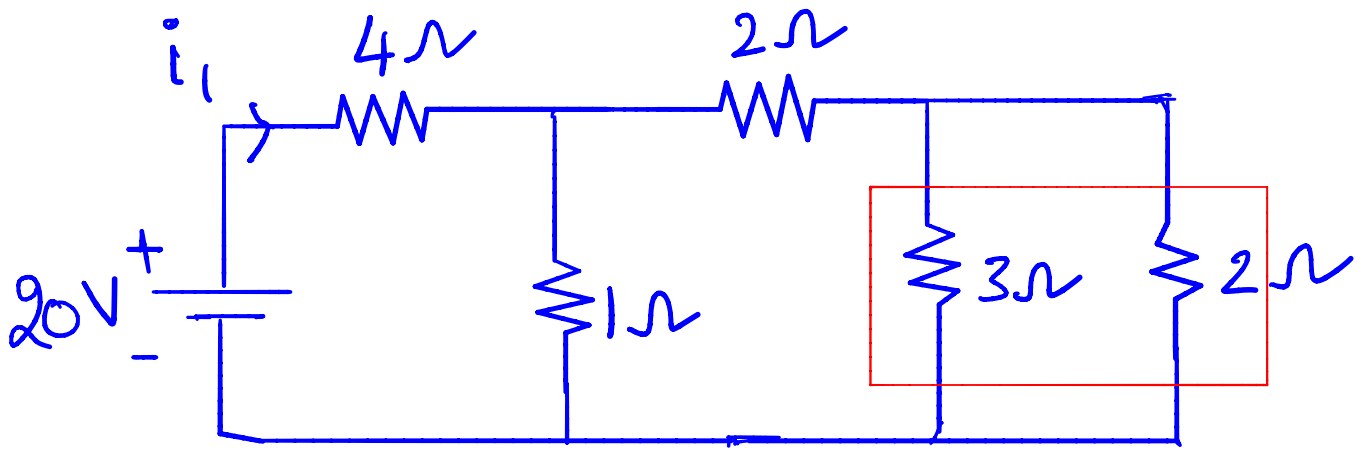


①

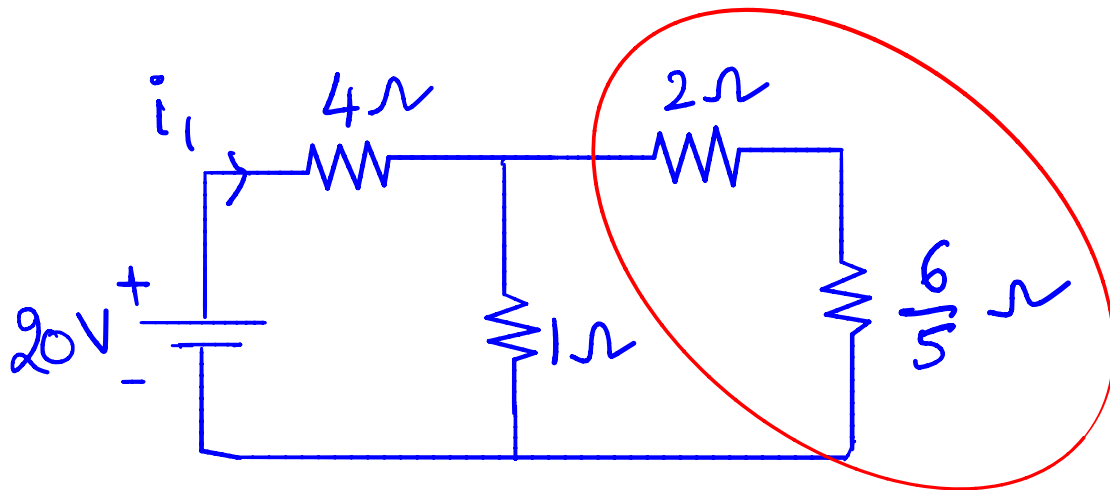


If  $R_1$  &  $R_2$  are in parallel then Equivalent resistance  $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

$$R_{equivalent} = \frac{3 \times 2}{3 + 2} = \frac{6}{5} \Omega$$




If  $R_1$  &  $R_2$  are in series then equivalent resistance  $R_{eq} = R_1 + R_2$

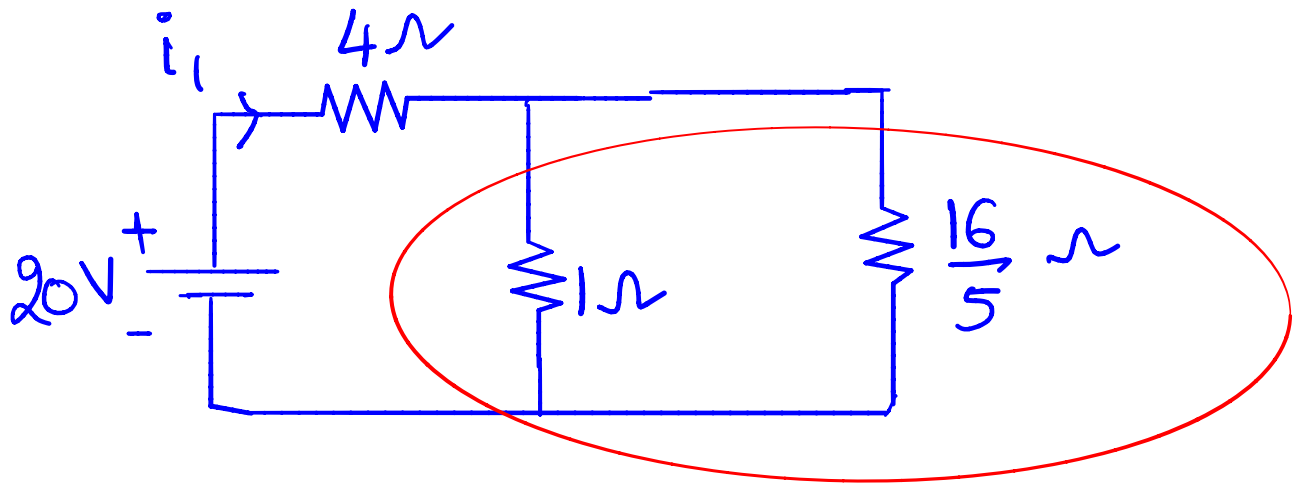
$$R_{eq} = 2 + \frac{6}{5} = \frac{16}{5} \Omega$$


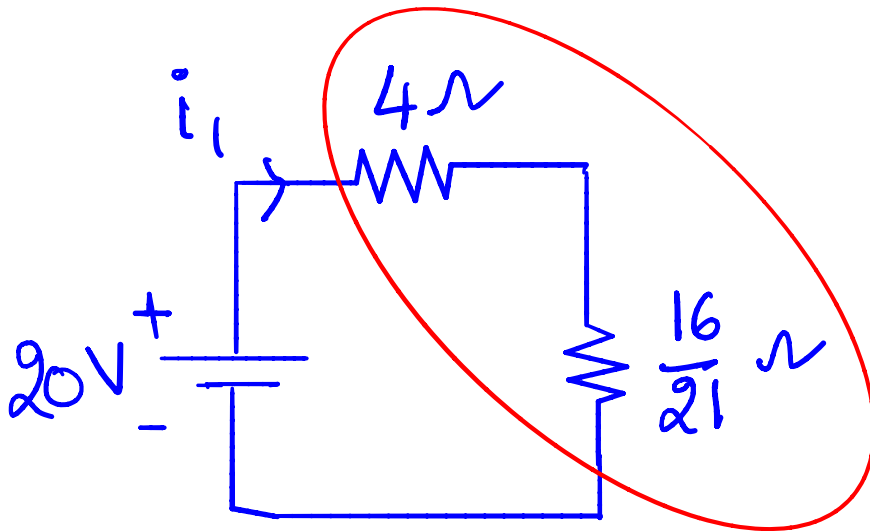
$$R_{eq} = \frac{1 \times \frac{16}{5}}{1 + \frac{16}{5}} = \frac{16}{21} \Omega$$


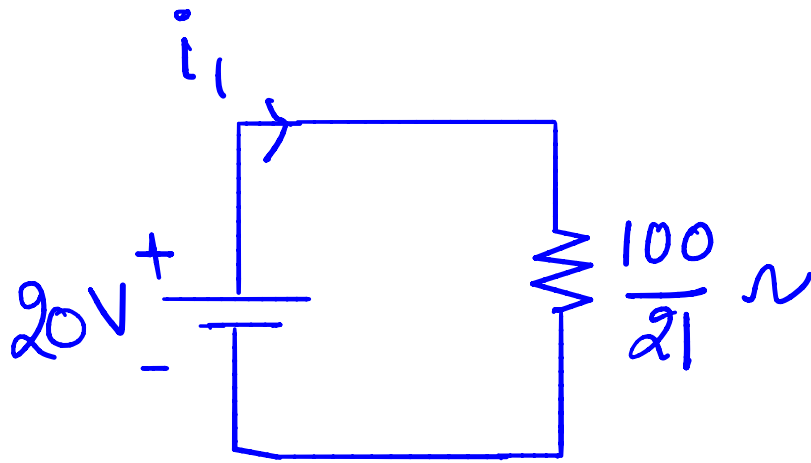
$$R_{eq} = 4 + \frac{16}{21} = \frac{100}{21}$$




By Ohm's Law,

$$i_1 = \frac{V}{R} = \frac{20}{\frac{100}{21}} = \frac{20 \times 21}{100}$$

$$\therefore i_1 = 4.2 \text{ A}$$

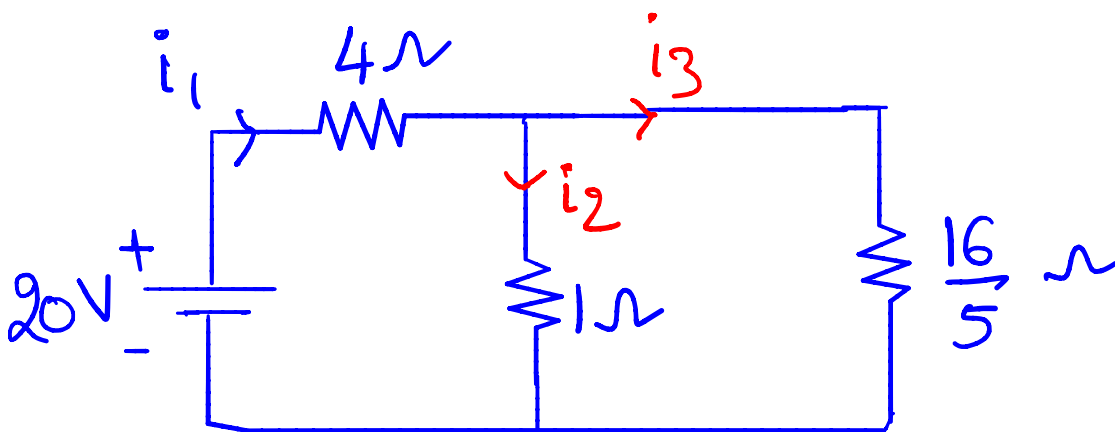② Let's draw the intermediate circuit in ① solution i.e



Let's denote  $i_2$  as current through  $1\Omega$  resistor

and  $i_3$  as current through  $\frac{16}{5} \Omega$  resistor.

$$\therefore \text{Current } i_2 = \frac{\frac{16}{5} \times i_1}{1 + \frac{16}{5}} \quad (i_1 = 4.2 \text{ A})$$

$$\therefore i_2 = \frac{16 \times 4.2}{21} = 3.2 \text{ A}$$


According KCL,

$$i_1 = i_2 + i_3$$

$$\therefore i_3 = i_1 - i_2 \\ = 4.2 - 3.2$$

$$i_3 = 1 \text{ A}$$

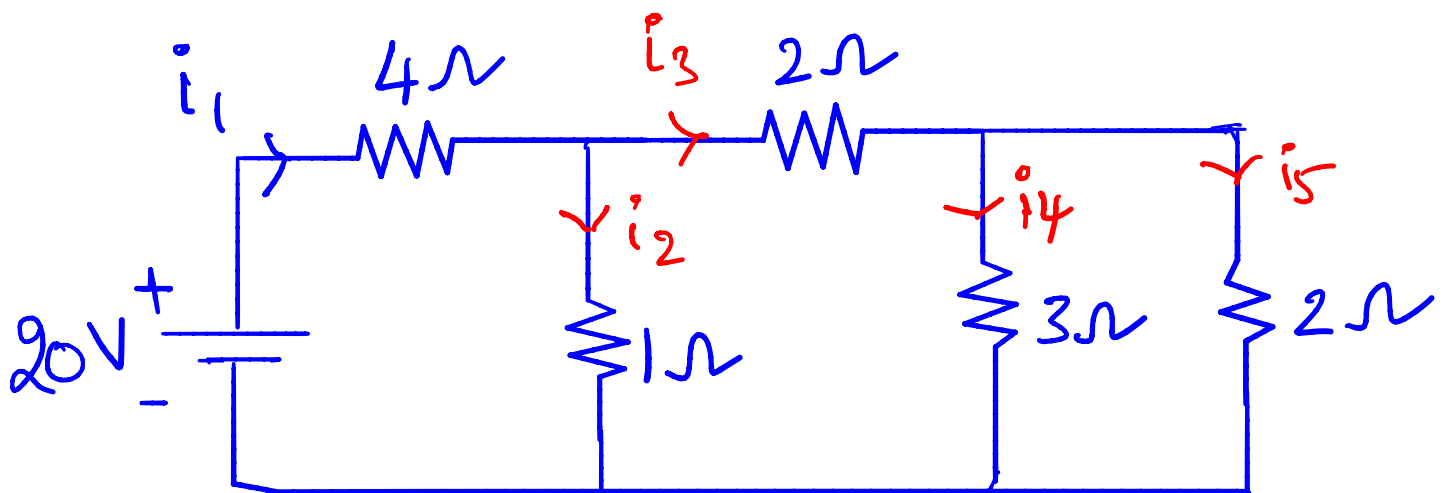Let's take circuit as and denote currents as



Current  $i_4$  can be calculated as

$$i_4 = \frac{2 \times i_3}{3+2} = \frac{2 \times 1}{5} = \frac{2}{5}$$


Current through  $3\Omega$  resistor =  $0.4\text{ A}$

Power dissipated in the resistor

$$= \frac{V^2}{R} = I^2 R$$

$\therefore$  Power dissipated in  $3\Omega$  Resistor
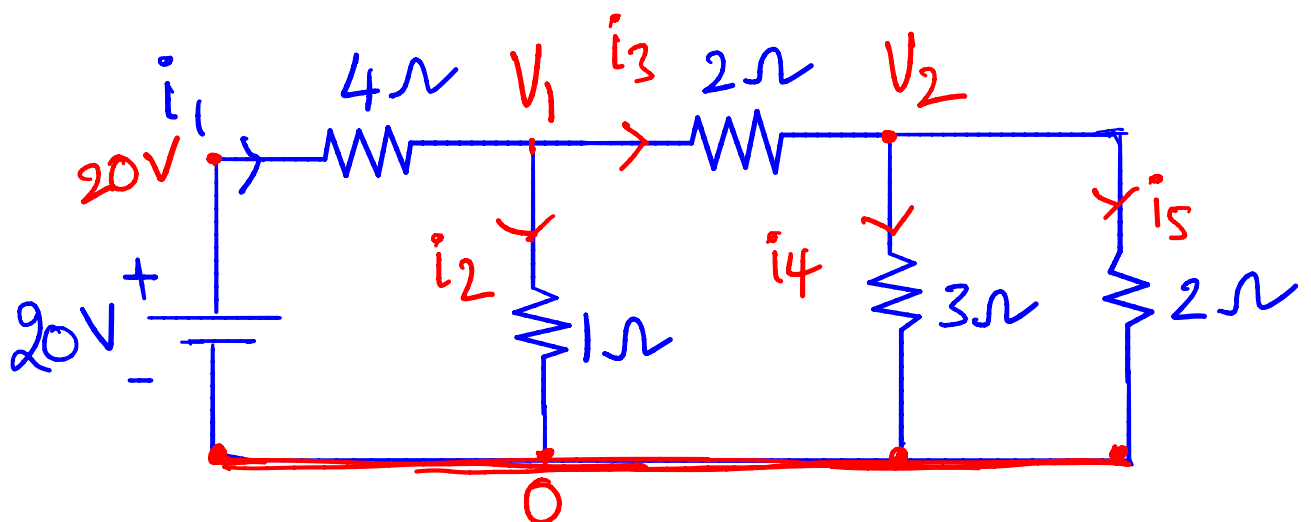
$$P_{3\Omega} = (0.4)^2 \times 3 = 0.48\text{ W}$$



In the above circuit 3 loops and 2 junctions are there.

$$i_1 = 4.2 \text{ A}$$

$$i_2 = 3.2 \text{ A}$$

$$i_3 = 1 \text{ A}$$

$$i_4 = 0.4 \text{ A}$$

$$i_5 = 0.6 \text{ A}$$

KVL at loop 1:

$$20 - i_1 \times 4 - i_2 \times 1 = 0$$

$$\Rightarrow 20 - 4.2 \times 4 - 3.2 = 0$$

$$\Rightarrow 20 - 20 = 0 \quad \checkmark$$

KVL satisfied.

KVL at loop 2:

$$i_3 \times 2 + i_4 \times 3 - i_2 \times 1 = 0$$

$$1 \times 2 + 0.4 \times 3 - 3.2 = 0$$

$$2 + 1.2 - 3.2 = 0$$

$$0 = 0 \quad \checkmark$$

KVL satisfied

KVL at loop 3 :

$$i_5 \times 2 - i_4 \times 3 = 0$$

$$0.6 \times 2 - 0.4 \times 3 = 0$$

$$1.2 - 1.2 = 0$$

$$0 = 0 \quad \checkmark$$

KVL satisfied

KCL

at  $V_1$  :

$$i_1 = i_2 + i_3$$

$$4.2 = 3.2 + 1 \Rightarrow 4.2 = 4.2 \quad \checkmark$$

at  $V_2$  :

$$i_3 = i_4 + i_5$$

$$1 = 0.4 + 0.6$$

$$1 = 1 \quad \checkmark$$

KCL, KVL are satisfied.